

Digital Logic Families


A Laxman
 Assistant Professor
 ECE Department

Overview

- Integration, Moore's law
- Early families (DL, RTL)
- TTL
- Evolution of TTL family
- ECL
- CMOS family and its evolution
- Overview


Integration Levels

 - Gate/transistor ratio is roughly 1/10
 - SSI < 12 gates/chip
 - MSI < 100 gates/chip
 - LSI ...1K gates/chip
 - VLSI ...10K gates/chip
 - ULSI ...100K gates/chip
 - GSI ...1Meg gates/chip



Moore's law

 
- A prediction made by Moore (a co-founder of Intel) in 1965: “... a number of transistors to double every 2 years.”



In the beginning...


Diode Logic (DL)

 - simplest; does not scale
- NOT not possible (need an active element)



Resistor-Transistor Logic (RTL)

 
- replace diode switch with a transistor switch
- can be cascaded
- large power draw



was...

Diode-Transistor Logic (DTL)

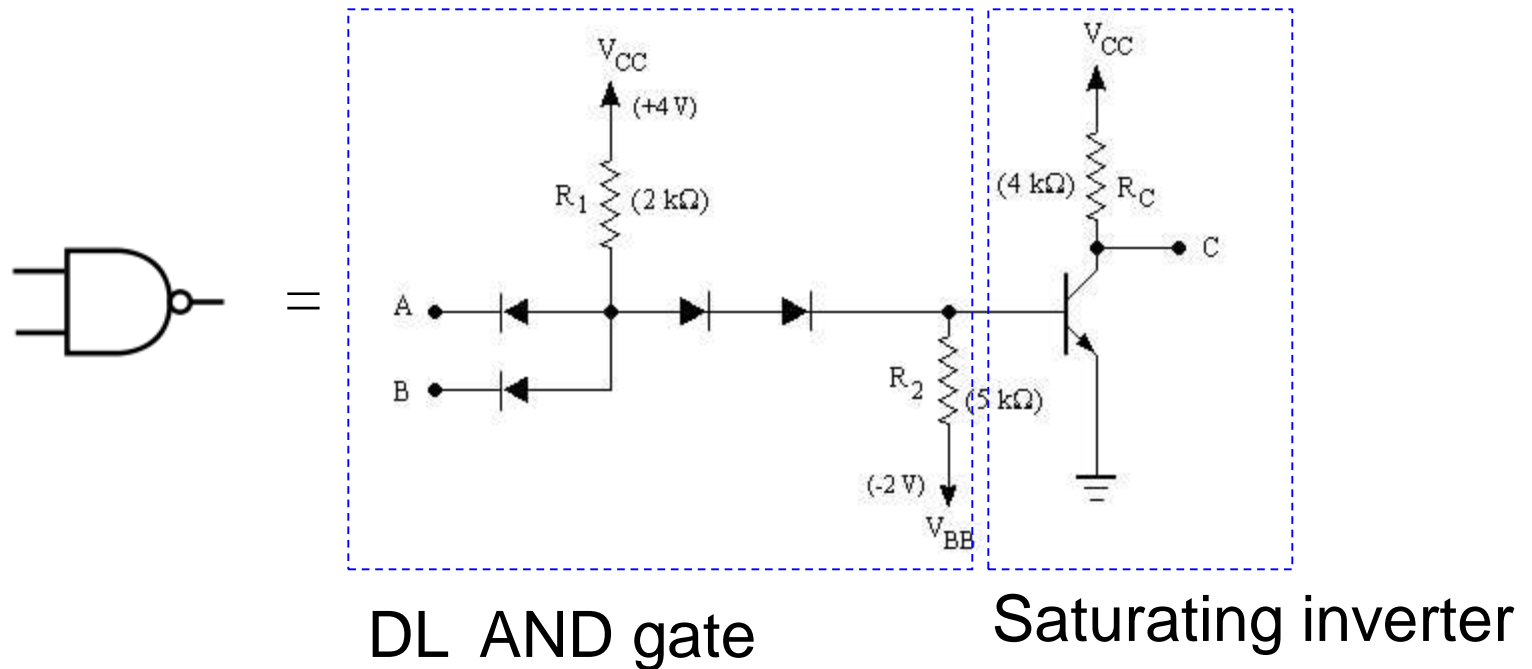- essentially diode logic with transistor amplification
- reduced power consumption
- faster than RTL




Logic families: V levels

$V_{OH}(\min)$ – The minimum voltage level at an output in the logical “1” state under defined load conditions

$V_{OL}(\max)$ – The maximum voltage level at an output in the logical “0” state under defined load conditions

$V_{IH}(\min)$ – The minimum voltage required at an input to be recognized as “1” logical state

 $V_{IL}(\max)$ – The maximum voltage required at an input that still will be recognized as “0” logical state




Logic families: I requirements

I_{OH} – Current flowing into an output in the logical “1” state under specified load conditions

I_{OL} – Current flowing into an output in the logical “0” state under specified load conditions


I_{IH} – Current flowing into an input when a specified HI level is applied to that input

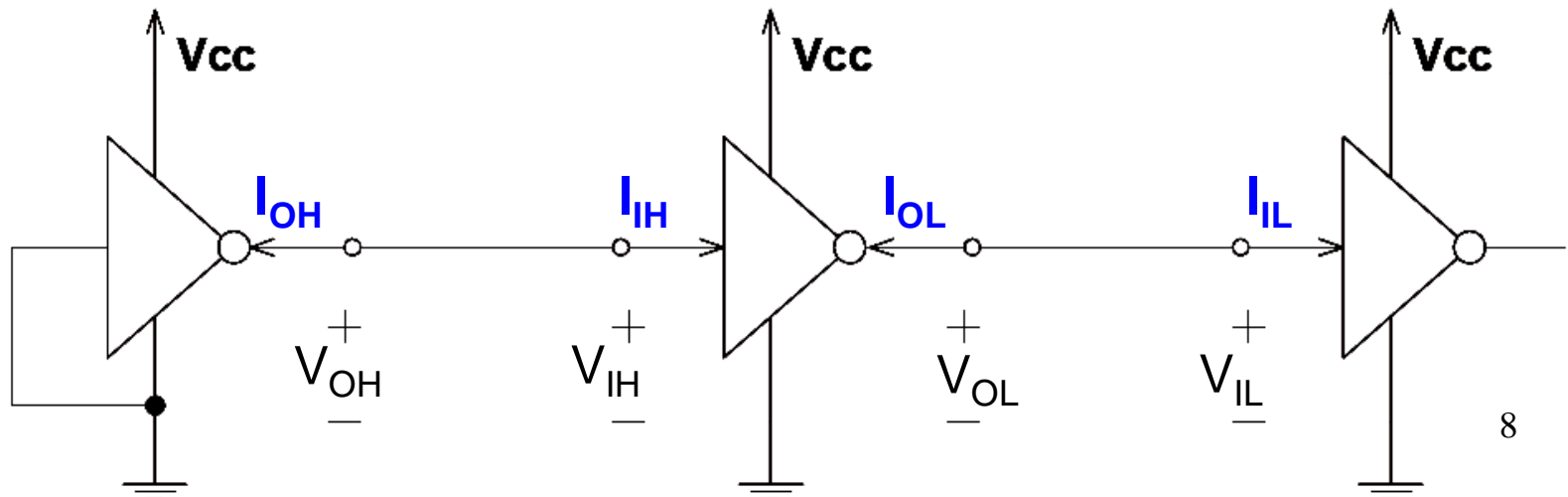I_{IL} – Current flowing into an input when a specified LO level is applied to that input




Logic families: fanout

 Fanout: the maximum number of logic inputs (of the same logic family) that an output can drive reliably



$$\text{DC fanout} = \min\left(\frac{I_{OH}}{I_{IH}}, \frac{I_{OL}}{I_{IL}}\right)$$

Logic families: propagation delay

 


$T_{PD,HL}$ – input-to-output propagation delay from HI to LO output

$T_{PD,LH}$ – input-to-output propagation delay from LO to HI output

Speed-power product: $T_{PD} \times P_{avg}$

Logic families: noise margin

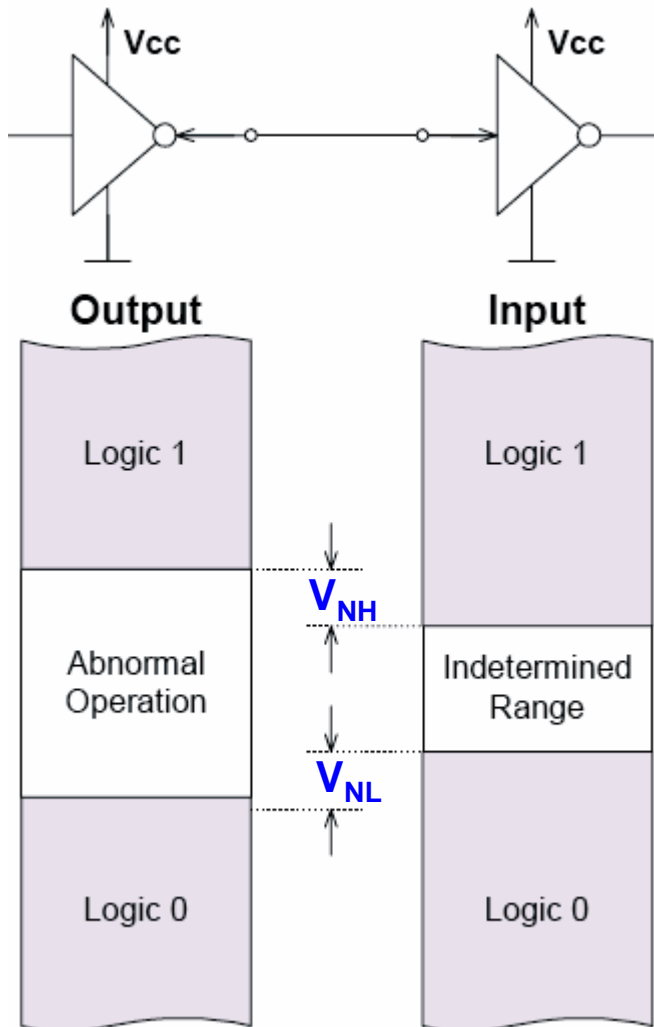

HI state noise margin:

$$V_{NH} = V_{OH}(\min) - V_{IH}(\min)$$

LO state noise margin:

$$V_{NL} = V_{IL}(\max) - V_{OL}(\max)$$

Noise margin:

$$V_N = \min(V_{NH}, V_{NL})$$


TTL

Bipolar Transistor-Transistor Logic (TTL)

- first introduced by in 1964 (Texas Instruments)
- TTL has shaped digital technology in many ways
- Standard TTL family (e.g. 7400) is obsolete
- Newer TTL families still used (e.g. 74ALS00)

Distinct features

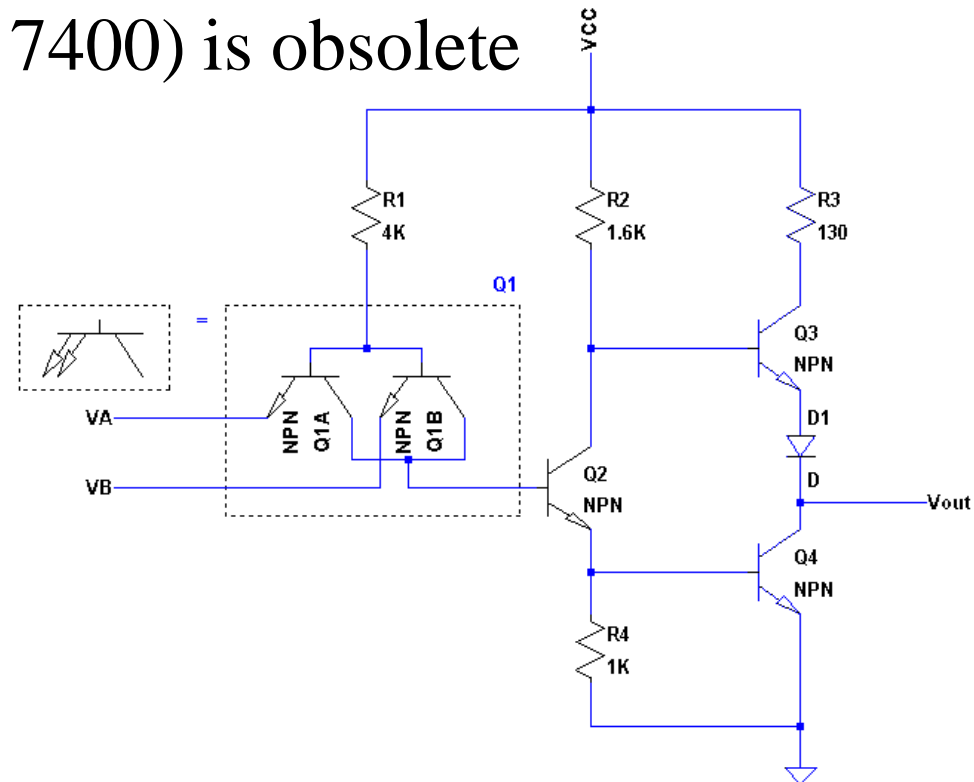- Multi-emitter transistors
- Totem-pole transistor arrangement
- Open LTspice example:
TTL NAND...



2-input NAND

ECL

Emitter-Coupled Logic (ECL)

- PROS: Fastest logic family available ($\sim 1\text{ns}$)
- CONS: low noise margin and high power dissipation
- Operated in emitter coupled geometry (recall differential amplifier or emitter-follower), transistors are biased and operate near their Q-point (never near saturation!)
- Logic levels. “0”: -1.7V . “1”: -0.8V
- Such strange logic levels require extra effort when interfacing to TTL/CMOS logic families.
- [Open LTspice example: ECL inverter...](#)

CMOS

Complimentary MOS (CMOS)

- Other variants: NMOS, PMOS (obsolete)
- Very low static power consumption
- Scaling capabilities (large integration all MOS)
- Full swing: rail-to-rail output
- Things to watch out for:
 - don't leave inputs floating (in TTL these will float to HI, in CMOS you get undefined behaviour)
 - susceptible to electrostatic damage (finger of death)
- Open LTspice example: CMOS NOT and NAND...

CMOS/TTL power requirements

- TTL power essentially constant (no frequency dependence)


- CMOS power scales as $\propto f \times C \times V^2$

frequency eff. capacitance supply volt.

- At high frequencies (\gg MHz) CMOS dissipates more power than TTL
- Overall advantage is still for CMOS even for very fast chips – only a relatively small portion of complicated circuitry operates at highest frequencies



Transistors as Switches

 - We can view MOS transistors as **electrically controlled switches**
- Voltage at gate controls path from source to drain





CMOS Inverter

A	Y
0	
1	

  



CMOS Inverter

A	Y
0	
1	0

  


CMOS Inverter

A	Y
0	1
1	0

  

Life-cycle

 

Thank you